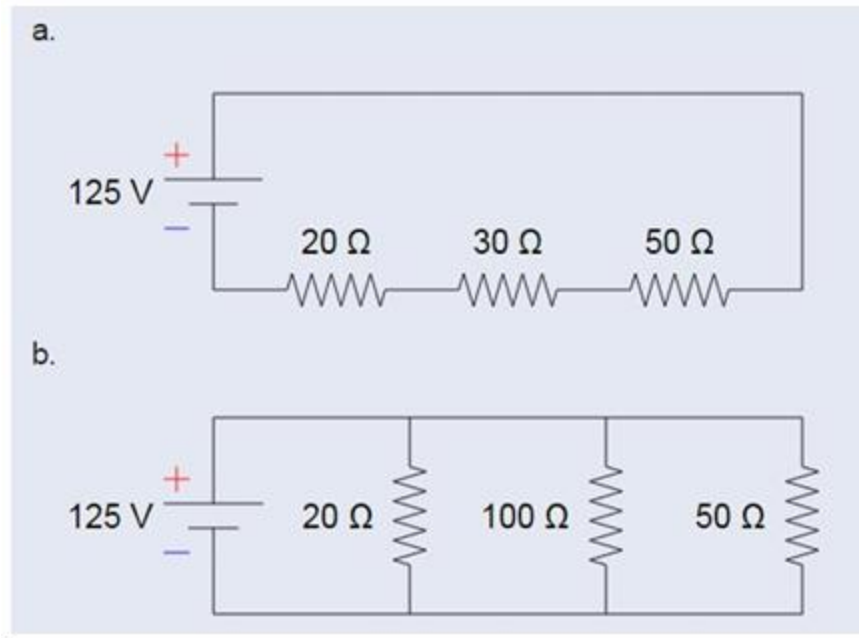


Practical Exercise 2: Circuit Design



Series Circuit

1. Calculate the total resistance in ohms,

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 20 + 30 + 50 \\ &= 100 \Omega \end{aligned}$$

2. Calculate the total current from the power supply

$$\begin{aligned} I &= V/R \\ &= \frac{125}{100} \\ &= 1.25 \text{ A} \end{aligned}$$

Current

3. Calculate the current through each resistor

Since it is in series, the current is the same

Current = 1.25 for all 3.

Practical Exercise 2: Circuit Design

4. Calculate the voltage drop through each resistor.

$$V = IR$$

$$\begin{aligned}\text{for } 20 \Omega &= 1.25 \times 20 \\ &= 25 \text{ V}\end{aligned}$$

$$\begin{aligned}30 \Omega &= 1.25 \times 30 \\ &= 37.5 \text{ V}\end{aligned}$$

$$\begin{aligned}50 \Omega &= 1.25 \times 50 \\ &= 62.5 \text{ V}\end{aligned}$$

5. Calculate the power dissipated through each resistor.

$$P = VI$$

$$\begin{aligned}\text{For } 20 \Omega &= 25 \times 1.25 \\ &= 31.25 \text{ W}\end{aligned}$$

$$\begin{aligned}30 \Omega &= 37.5 \times 1.25 \\ &= 46.875 \text{ W}\end{aligned}$$

$$\begin{aligned}50 \Omega &= 62.5 \times 1.25 \\ &= 78.125 \text{ W}\end{aligned}$$

Parallel Circuit

1. Total resistance

$$\begin{aligned}\frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{20} + \frac{1}{100} + \frac{1}{50} \\ &= 0.08 \\ R_T &= \frac{1}{0.08} \\ &= 12.5\end{aligned}$$

2. Total current from power supply

$$\begin{aligned}I_T &= \frac{V}{R_T} \\ &= \frac{125}{12.5} \\ &= 10 \text{ A}\end{aligned}$$

3. Current through each resistor

$$\begin{aligned}I &= V/R \\ &= 125/20 \\ &= 6.25 \text{ A}\end{aligned} \quad \left. \vphantom{\begin{aligned} I &= V/R \\ &= 125/20 \\ &= 6.25 \text{ A} \end{aligned}} \right\} \text{ For } 20\Omega$$

$$\begin{aligned}\text{For } 100\Omega &= 125/100 \\ &= 1.25 \text{ A}\end{aligned}$$

$$50\Omega = 125/50 = 2.5 \text{ A}$$

Practical Exercise 2: Circuit Design

4. Voltage drop through each resistor

Voltage is same across
 $V = 12.5V$

5. Power dissipated through each resistor

$$P = VI$$

$$\begin{aligned}\text{For } 20\Omega &= 12.5 \times 6.25 \\ &= 781.25 \text{ W}\end{aligned}$$

$$\begin{aligned}100\Omega &= 12.5 \times 1.25 \\ &= 156.25 \text{ W}\end{aligned}$$

$$\begin{aligned}50\Omega &= 12.5 \times 2.5 \\ &= 312.5 \text{ W}\end{aligned}$$